



Prof. Dr. Florian Künzner


Technical University of Applied Sciences Rosenheim, Computer Science

Start: 8:01

CA 3 – Logical hardware

The lecture is based on the work and the documents of Prof. Dr. Theodor Tempelmeier

Goal

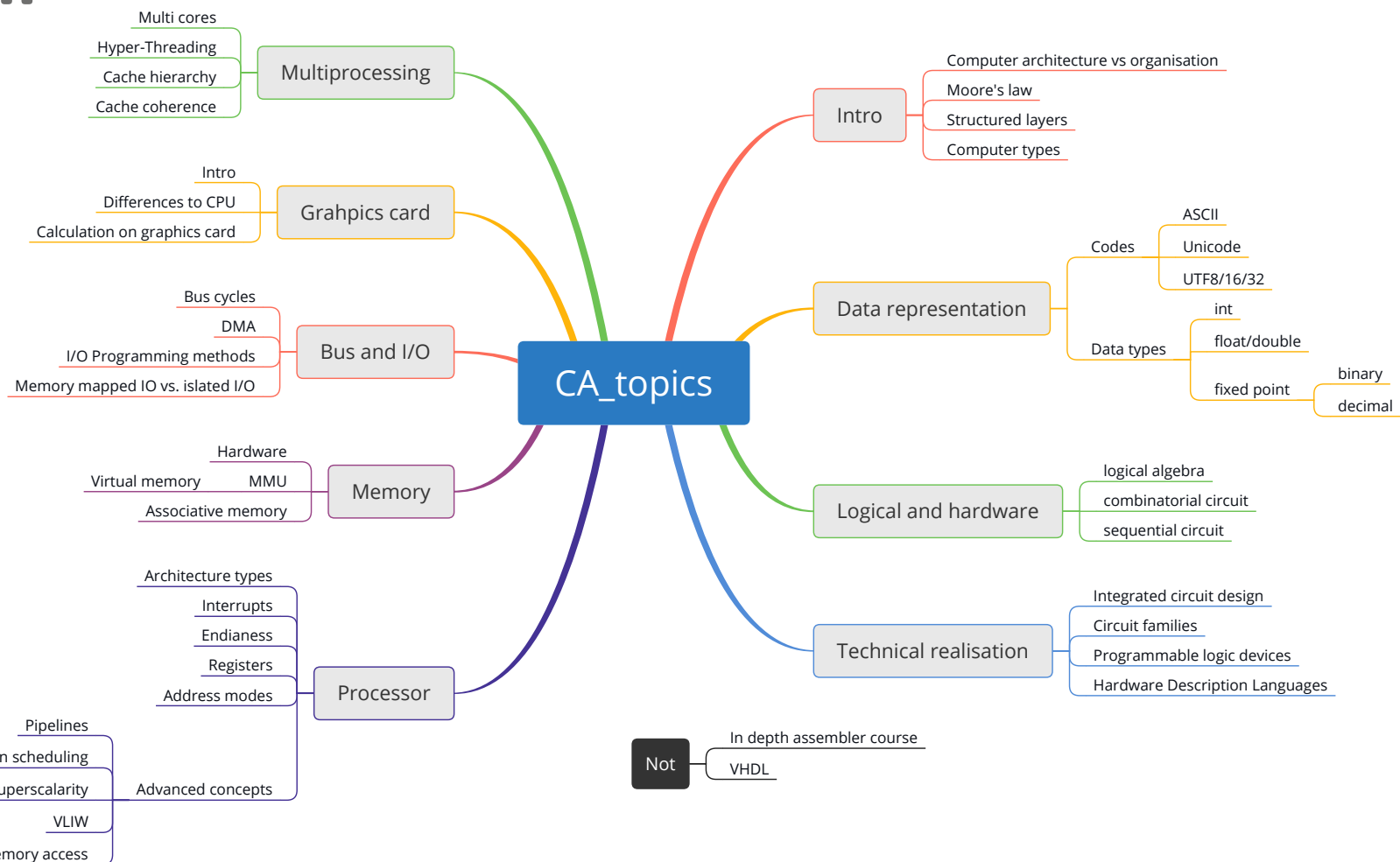

Goal

CA::Logical hardware

- Logical algebra
- Logical elements
- Combinatorial circuits
- Sequential circuits

Logical algebra

Notation:

Logical algebra

Notation:

Operators $\vee, +, OR$ \wedge, \cdot, AND \neg, \bar{x}, NOT

Logical algebra

Notation:

Operators $\vee, +, OR$ \wedge, \cdot, AND \neg, \bar{x}, NOT

Operand $\{0, 1\}$

Axiom	$a + b = b + a$	$a \cdot b = b \cdot a$
	$(a + b) + c = a + (b + c)$	$(a \cdot b) \cdot c = a \cdot (b \cdot c)$
	$a + (a \cdot b) = a$	$a \cdot (a + b) = a$
	$a + 0 = a$	$a \cdot 1 = a$
	$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$	$a + (b \cdot c) = (a + b) \cdot (a + c)$
	$a \cdot \neg a = 0$	$a + \neg a = 1$

Logical algebra

Notation:

Operators $\vee, +, OR$ \wedge, \cdot, AND \neg, \bar{x}, NOT

Operand $\{0, 1\}$

Axiom $a + b = b + a$

$a \cdot b = b \cdot a$

$(a + b) + c = a + (b + c)$ $(a \cdot b) \cdot c = a \cdot (b \cdot c)$

$a + (a \cdot b) = a$ $a \cdot (a + b) = a$

$a + 0 = a$ $a \cdot 1 = a$

$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$ $a + (b \cdot c) = (a + b) \cdot (a + c)$



$a \cdot \neg a = 0$ $a + \neg a = 1$

De Morgan $\neg(a \cdot b) = \neg a + \neg b$ $\neg(a + b) = \neg a \cdot \neg b$





Logical elements

Type New DIN norm American norm

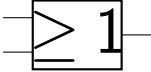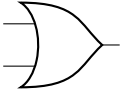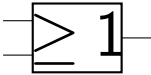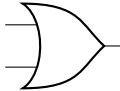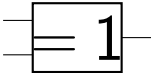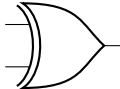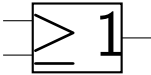
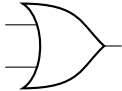
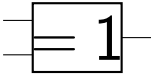
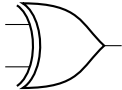

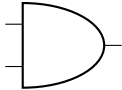
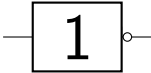
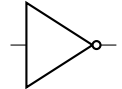


Logical elements

Type	New DIN norm	American norm
OR		

Logical elements

Type	New DIN norm	American norm
OR		
XOR		


Logical elements

Type	New DIN norm	American norm
OR		
XOR		
AND		
Invert		
		



Combinatorial circuits

 A combination of logical elements into a circuit.




- Switching function = logical combinations
- Representation by truth tables or boolean expressions



Combinatorial circuits

 A combination of logical elements into a circuit.




- Switching function = logical combinations
- Representation by truth tables or boolean expressions



Combinatorial circuits

 A combination of logical elements into a circuit.



- Switching function = logical combinations
- Representation by truth tables or boolean expressions

Sequential circuits

Definition

Sequential circuits = combinational circuit + clock pulse + internal states

- Through the clock pulse it is a clocked (getaktete) operation mode
- Internal states (e.g. through flip-flop registers)

Sequential circuits

Definition

Sequential circuits = combinational circuit + clock pulse + internal states

- Through the clock pulse it is a clocked (getaktete) operation mode
- Internal states (e.g. through flip-flop registers)

Sequential circuits

Definition


Sequential circuits = combinational circuit + clock pulse + internal states

- Through the clock pulse it is a clocked (getaktete) operation mode
- Internal states (e.g. through flip-flop registers)



Sequential circuits

 A combinational circuit with a clock pulse.




- Flip-flop registers at input and output (I/O registers)
- Clock pulse for transfer data at a defined time



Sequential circuits

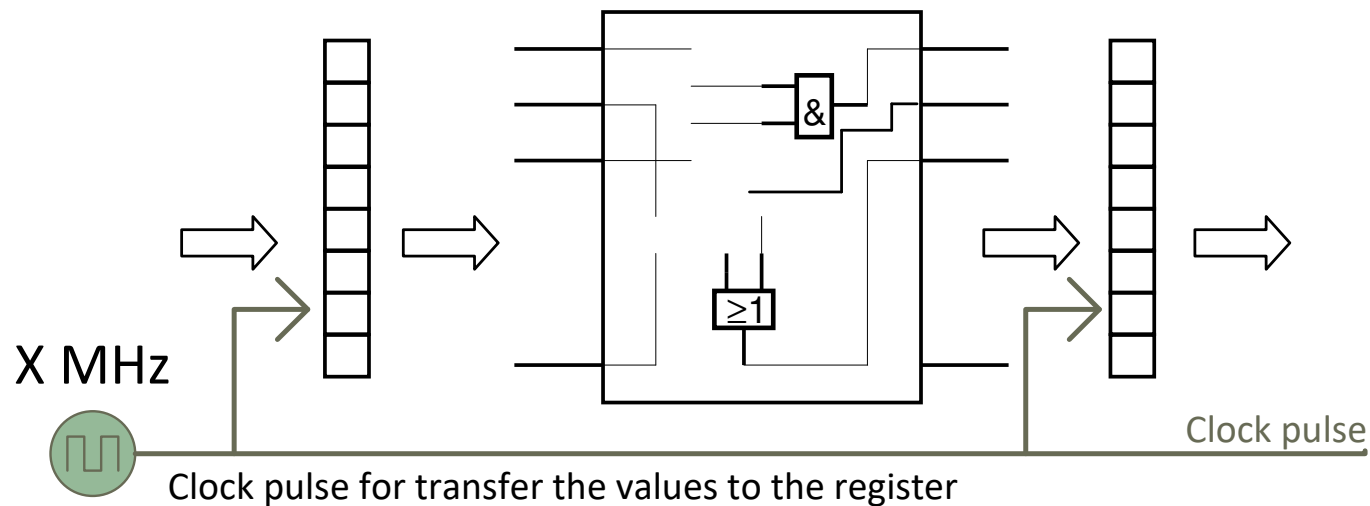A combinational circuit with a clock pulse.




- Flip-flop registers at input and output (I/O registers)
- Clock pulse for transfer data at a defined time



Sequential circuits

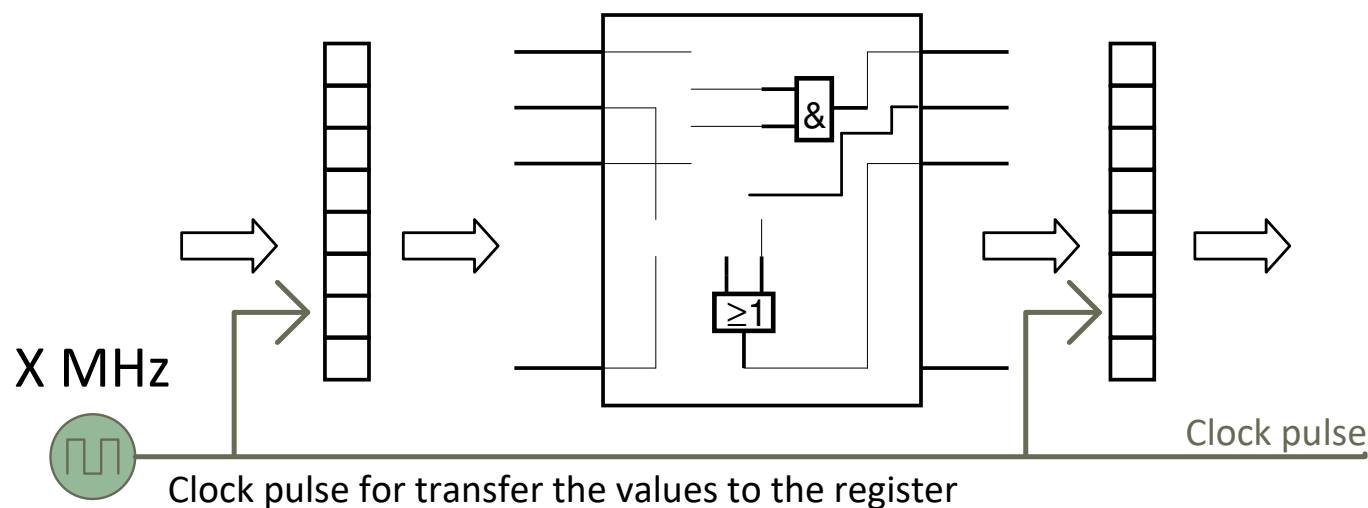A combinational circuit with a clock pulse.



- Flip-flop registers at input and output (I/O registers)
- Clock pulse for transfer data at a defined time

Sequential circuits

Also called synchronous circuits:

- Theoretically divided into combinational circuit and memory elements (registers).
- It takes t_{max} time until all signals are through the network of logic elements.
- Signals are only transferred to memory elements (I/O registers) at defined clock times (clock pulse).

Condition

$$\frac{1}{\text{clock rate (frequency)}} > t_{max} \quad (1)$$

If you want higher clock rate $\Rightarrow t_{max}$ has to be reduced:

- Improvements in electrical engineering and solid state physics
- Redesign of circuit with less logic elements

Sequential circuits

Also called synchronous circuits:

- Theoretically divided into combinational circuit and memory elements (registers).
- It takes t_{max} time until all signals are through the network of logic elements.
- Signals are only transferred to memory elements (I/O registers) at defined clock times (clock pulse).

Condition

$$\frac{1}{\text{clock rate (frequency)}} > t_{max} \quad (1)$$

If you want higher clock rate $\Rightarrow t_{max}$ has to be reduced:

- Improvements in electrical engineering and solid state physics
- Redesign of circuit with less logic elements

Sequential circuits

Also called **synchronous circuits**:

- Theoretically divided into combinational circuit and memory elements (registers).
- It takes t_{max} time until all signals are through the network of logic elements.
- Signals are only transferred to memory elements (I/O registers) at defined clock times (clock pulse).

Condition

$$\frac{1}{\text{clock rate (frequency)}} > t_{max} \quad (1)$$

If you want higher clock rate $\Rightarrow t_{max}$ has to be reduced:

- Improvements in electrical engineering and solid state physics
- Redesign of circuit with less logic elements

Sequential circuits

Also called **synchronous circuits**:

- Theoretically divided into combinational circuit and memory elements (registers).
- It takes t_{max} time until all signals are through the network of logic elements.
- Signals are only transferred to memory elements (I/O registers) at defined clock times (clock pulse).

Condition

$$\frac{1}{\text{clock rate (frequency)}} > t_{max} \quad (1)$$

If you want higher clock rate $\Rightarrow t_{max}$ has to be reduced:

- Improvements in electrical engineering and solid state physics
- Redesign of circuit with less logic elements

Sequential circuits

Also called **synchronous circuits**:

- Theoretically divided into combinational circuit and memory elements (registers).
- It takes t_{max} time until all signals are through the network of logic elements.
- Signals are only transferred to memory elements (I/O registers) at defined clock times (clock pulse).

Condition

$$\frac{1}{\text{clock rate (frequency)}} > t_{max} \quad (1)$$

If you want higher clock rate $\Rightarrow t_{max}$ has to be reduced:

- Improvements in electrical engineering and solid state physics
- Redesign of circuit with less logic elements

Sequential circuits

Also called **synchronous circuits**:

- Theoretically divided into combinational circuit and memory elements (registers).
- It takes t_{max} time until all signals are through the network of logic elements.
- Signals are only transferred to memory elements (I/O registers) at defined clock times (clock pulse).

Condition

$$\frac{1}{\text{clock rate (frequency)}} > t_{max} \quad (1)$$

If you want higher clock rate $\Rightarrow t_{max}$ has to be reduced:

- Improvements in electrical engineering and solid state physics
- Redesign of circuit with less logic elements

Questions?

All right?



Question?



and use **chat**

or

speak *after* I
ask you to

Summary and outlook

Summary

- Logical algebra
- Logical elements
- Combinatorial circuits
- Sequential circuits

Outlook

- Technical realisation

Summary and outlook

Summary

- Logical algebra
- Logical elements
- Combinatorial circuits
- Sequential circuits

Outlook

- Technical realisation