



## Exercise sheet 3 – Hardware

### Goals:

- Basic knowledge about chip manufacturing
- Hardware circuits
- Interrupt handling

### Exercise 3.1: Chip manufacturing?

We'll watch the *chip manufacturing* video from Infineon: [https://www.youtube.com/watch?v=\\_Kj58yQ67KI](https://www.youtube.com/watch?v=_Kj58yQ67KI)

- (a) What is the main commodity for computer chips.

**Proposal for solution:** Sand/Silicium.

- (b) What is a transistor in the context of a microchip and how many pins does it have?

**Proposal for solution:** A transistor is the smallest switch unit on a microchip. Every transistor has 3 pins. It works like a switch.

- (c) How are the chips designed/programmed/planned?

**Proposal for solution:** With computer aided design (CAD) and simulation programs.

- (d) What kind of production environment is required to produce computer chips?

**Proposal for solution:** A special clean room (dust-free) is required.

- (e) How many chips can be produced on a wafer?

**Proposal for solution:** Some dozen up to several thousand, depending on the wafer size and the chip size.

- (f) How many pins does each chip have?

**Proposal for solution:** More than 1000 pins are possible.

### Exercise 3.2: Update RA repository

- (a) `cd RA_exercises`  
(b) `git pull`

### Exercise 3.3: Hardware: combinatorial circuit vs. sequential circuit?

- (a) Describe the difference between combinatorial circuits and sequential circuits.

**Proposal for solution:** sequential circuit = combinatorial circuit + time (clock) + register states

- sequential circuit = Schaltwerk
- combinatorial circuit = Schaltnetz


- (b) The programmable logic device (PLD) *GAL 16v8* can be run in 'simple mode' without a clock entry or in 'registered mode' with clock entry (cf. [RA\\_exercises/sheet\\_03/lattice\\_gal16v8.pdf](#)). State the reference to the question 3.3a.

### Exercise 3.4: Hardware: GAL Programming

For this exercise use the [RA\\_exercises/sheet\\_03/gal16v8\\_logic\\_diagram\\_registered\\_mode.pdf](#) file as a template for your drawings (programming). Program the GAL16V8 in **registered mode**. *Hint: You may print this or you use a PDF annotator like Xournal++.*

- (a) Denote the clock input as:  $CLK$ .
- (b) Denote the inputs as:  $A_0, A_1, \dots$
- (c) Denote the outputs as:  $Q_0, Q_1, \dots$
- (d) Program  $Q_0 = \bar{A}_2 + A_7$
- (e) Program  $Q_1 = A_3 \cdot \bar{A}_2 \cdot A_1 \cdot \bar{A}_0 + A_3 \cdot A_4 \cdot \bar{A}_5 + A_6$
- (f) Program  $Q_2 = A_7$
- (g) Program  $Q_3 = A_6 \cdot A_3 \cdot Q_0 + \bar{Q}_2$

**Proposal for solution:**

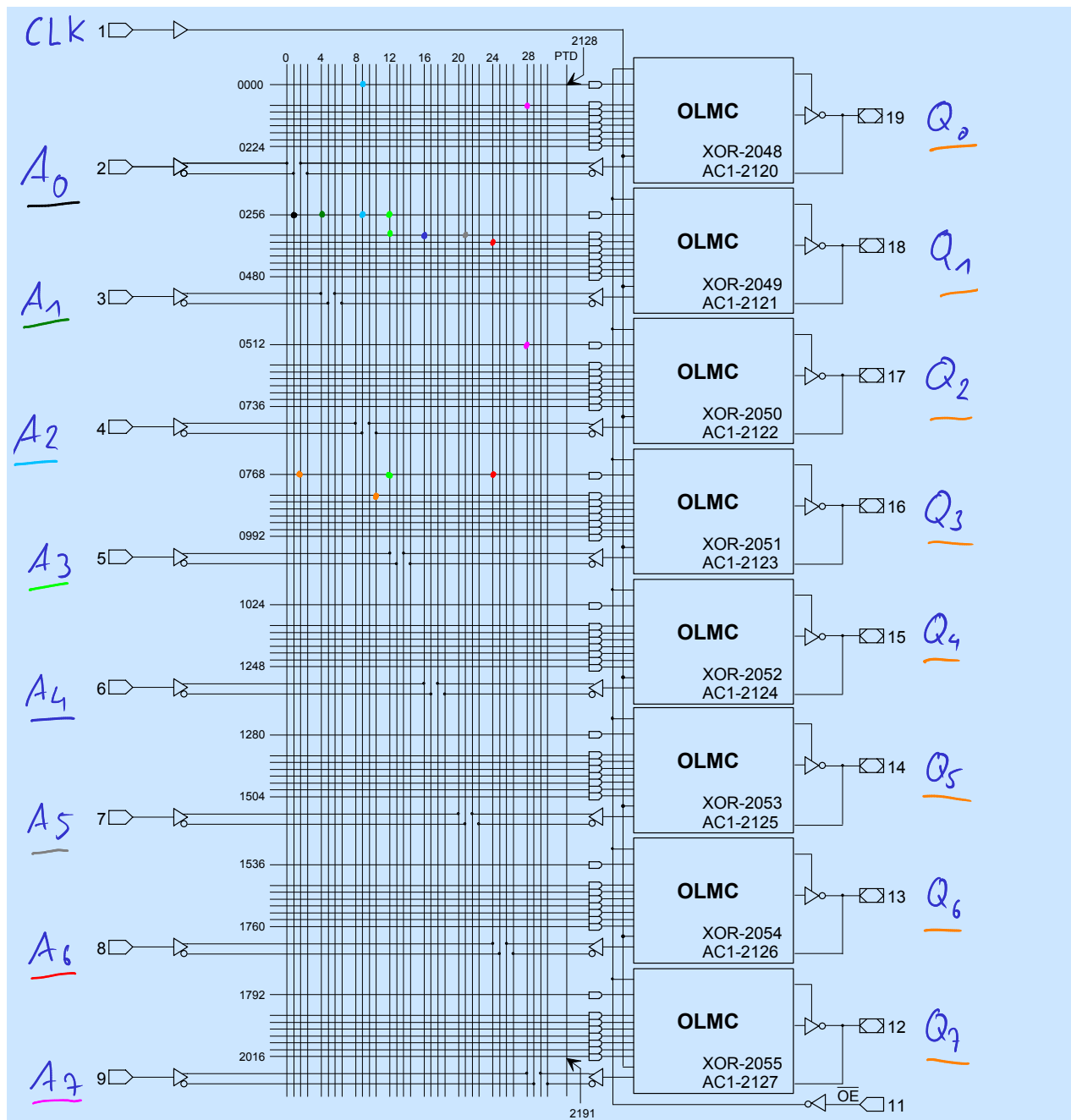

### Exercise 3.5: Signal propagation time of the Lattice GAL16V8

- (a) The Lattice GAL16V8 has a maximum signal propagation time of  $t_{max} = 3.5$  ns. What is the supported theoretical maximum frequency  $F_{max}$  in MHz?

**Proposal for solution:**  $F_{max} \approx 285$  MHz. The GAL16V8 documentation states  $F_{max} = 250$  MHz, this is a bit slower than the theoretical maximum frequency which we calculated, due to some more detailed timing delays that has to be considered.